
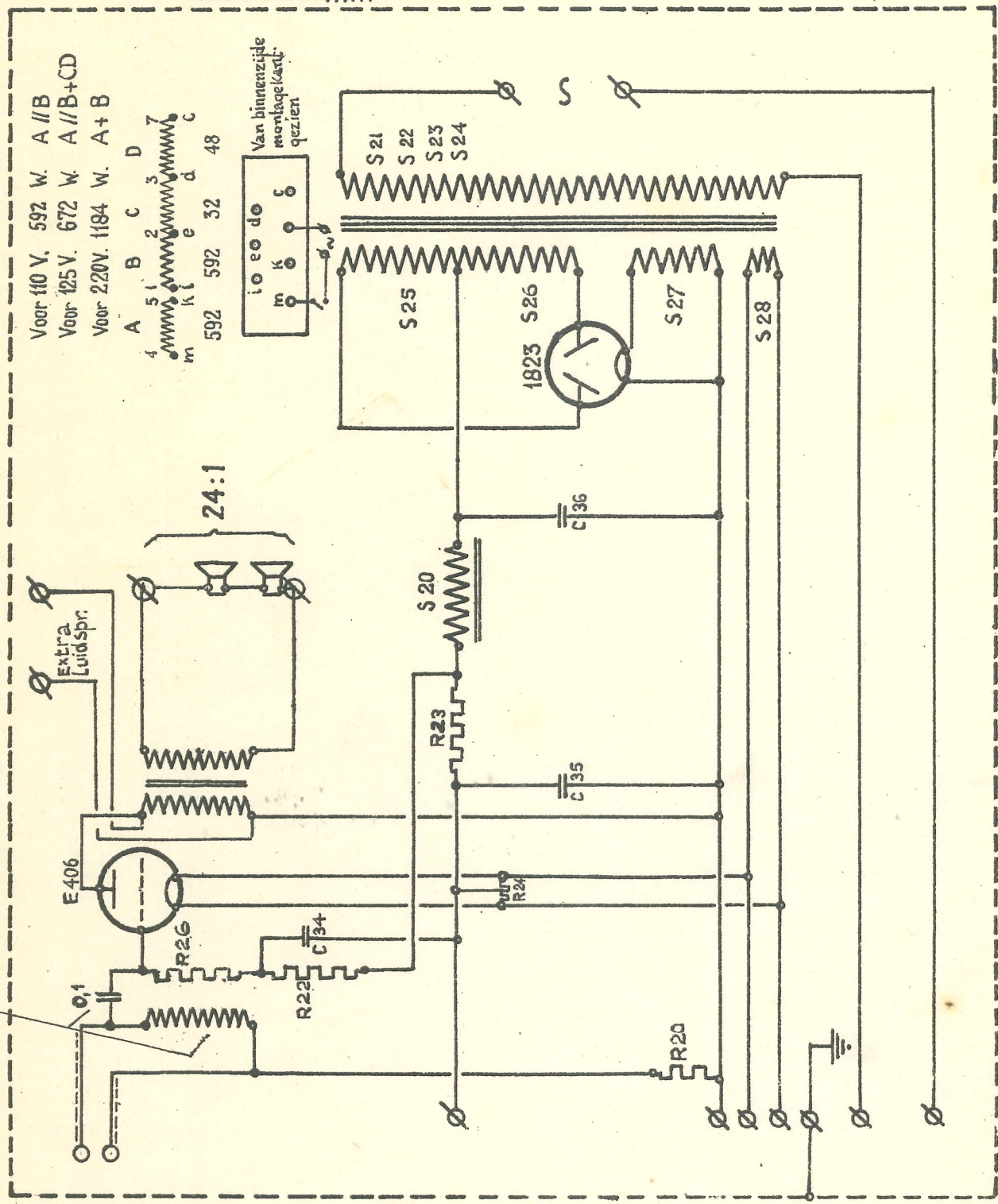


Auteursrecht volgens de wet voorbehouden

Titel: ONTVANG.GEDEELTE KY 121	Opmerkingen: Voor weerstanden en condensatoren zie teek. 2034.	A 4
 N.V. Radiofabriek en Ingenieursbureau v/h VAN DER HEEM en BLOEMSMA	25 = ± 0,5 25,0 = ± 0,2 25,0 = ± 0,05	Schaal: / Get. Meester 1/9 '32 Gez.
		25114070 25114070 25114331

2033

L.S. FILTER 25114930






Voor 110 V. 592 W. A // B
 Voor 125 V. 672 W. A // B + CD
 Voor 220 V. 1184 W. A + B

A 5 1 2 3 4
 B 1 2 3 4
 C 1 2 3 4
 D 1 2 3 4


4 5 1 2 3 4
 m k l e d c

592 592 32 48

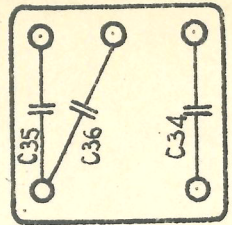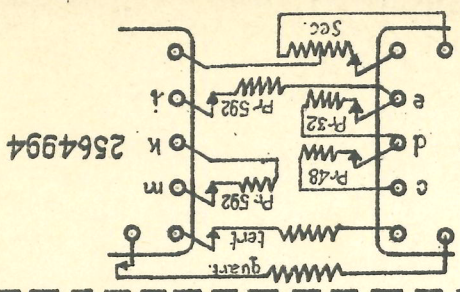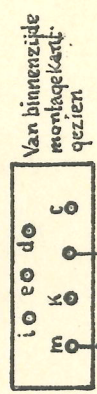

25115890

Auteursrecht volgens de wet voorbehouden

Titel: P. S. A. K U 121	Opmerkingen: <i>condensatoren, weerstanden 2034 omv. aangegeven → 2033</i>	A 4		
 N.V. Radiofabriek en Ingenieursbureau v/h VAN DER HEEM en BLOEMSMA	25 = ± 0,5 25,0 = ± 0,2 25,0 = ± 0,05	Schaal: Gecalq. Π	Get. Π <i>pesters 5/9 '32</i> Gez.	2037

C 1	80 $\mu\mu\text{F}$	C 29	1000 $\mu\mu\text{F}$	R 1	$\rightarrow 1 \text{ M } \Omega$
C 2	32 $\mu\mu\text{F}$	- C 30	4 μF	R 2	2 x 15000 Ω
C 3	630 ..	- C 31	0,5 μF	R 3	40000 Ω
C 4	9 ..	- C 32	1,5 μF	R 4	50000 Ω
C 5	27 ..	- C 33	1 μF	R 5	20000 Ω
C 6	27 ..	- C 34	2 μF	R 6	1 M Ω
C 7	9 ..	- C 35	4 μF	R 7	400 Ω
C 8	630 ..	- C 36	4 μF	R 8	400 Ω
C 9	0,5 μF	C 37	50000 $\mu\mu\text{F}$	R 9	50000 Ω
C10	0,5 ..			R 10	40000 Ω
C11	0,5 ..			R 11	20000 Ω
C12	27 $\mu\mu\text{F}$			R 12	0,2 M Ω — 22-12-32
C13	9 ..			R 13	0,2 M Ω — "
C14	630 ..			R 14	2 x 10000 Ω
C15	50000 ..			R 15	100000 Ω
C16	50000 ..			R 16	20000 Ω
C17	50000 ..			R 17	0,64 M Ω
C18	50000 ..			R 18	0,2 M Ω
C19	125 ..			R 19	0,2 M Ω
C20	0,5 μF			R 20	32000 Ω
C21	800 $\mu\mu\text{F}$			R 21	50 Ω
C22	0,5 μF			R 22	20000 Ω
C23	50000 $\mu\mu\text{F}$			R 23	650 Ω
C24	125 $\mu\mu\text{F}$			R 24	2 x 120 Ω
C25	3 μF			R 25	100000 Ω
C26	500 $\mu\mu\text{F}$			R 26	25000 Ω — 22-12-32
C27	200 $\mu\mu\text{F}$			R 27	10000 Ω — "
C28	200 ..				

Auteursrecht volgens de wet voorbehouden

Titel: Condensatoren en weerstanden
K IJ 121

Opmerkingen: Behoort bij teek 2033

A 4



N.V. Radiofabriek en Ingenieursbureau v/h
VAN DER HEEM en BLOEMSMA

25 = $\pm 0,5$
25,0 = $\pm 0,2$
25,0 = $\pm 0,05$

Schaal:

Gecalq.

Get. 17/9 '32

Gez.

2034